


Date: \_\_\_\_\_

Name: \_\_\_\_\_
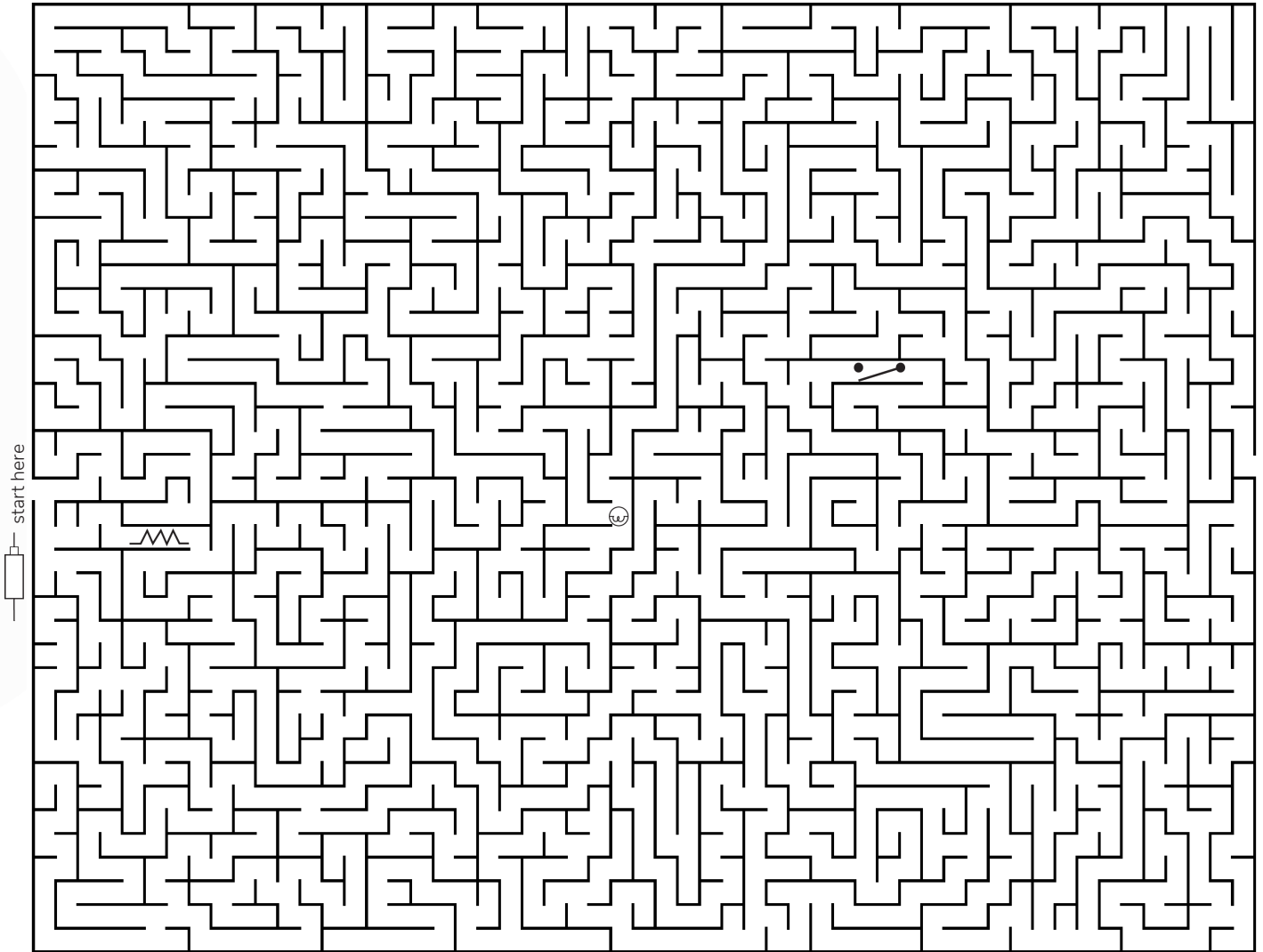
## Electricity Maze

This activity was created by Reem.

Find your way through the maze and collect the pieces for the circuit along the way! Then draw the complete circuit with pieces you collected below. Start with the battery.



Draw the circuit here: